


$$1 - A = x'y'z + x'yz' + xy'$$

- a) Minimize A (using Karnaugh Map)
- b) Convert this minimized function to a digital circuit.
- c) Implement the function A by using 3x8 decoder.

a)

	$x \setminus y \setminus z$	00	01	11	10	\sum
0		0	1	0	1	
$x \setminus$	1	1	1	0	0	$\sum z$

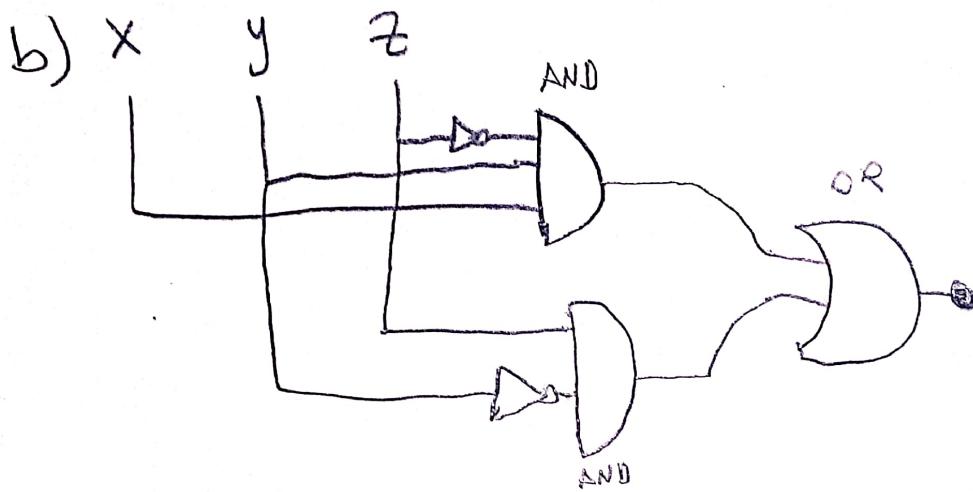$A = \bar{z} \cdot y' + x \cdot y \cdot z'$



I hereby pledge on my honor that I will not give/receive any info from/to anybody. The work I done is solely my own.


Süleyman Gölbel

1801042656

~~SK~~

CSE 232 Final
Group 5

c)

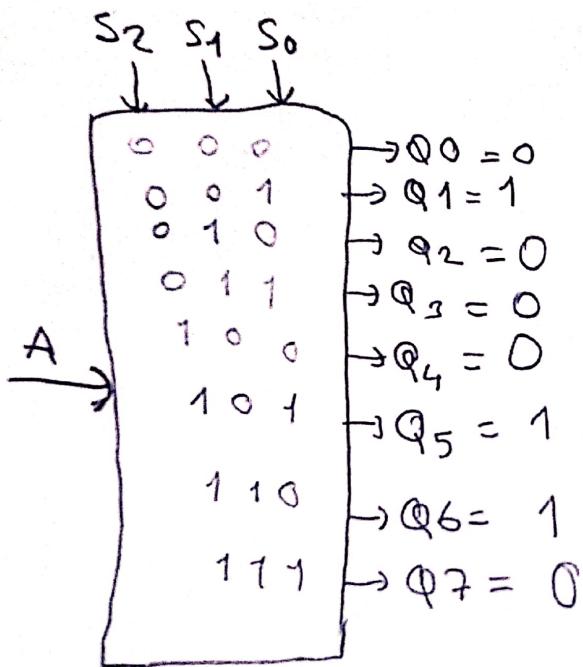

3x8 decoder

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0